

Logic Circuit

Boolean Variables

- A Boolean Variable takes the value of either 0 or 1.
- In digital electronics, Boolean 0 and 1 correspond to binary 0 and 1.
- In logic, 0 and 1 are sometimes called FALSE and TRUE.
- We use symbols to represent Boolean variables.

E.g.: A, B, C, X, Y, Z.

Logic Gate

- A logic gate is an elementary building block of a digital circuit .
- Most logic gates have two inputs and one output. At any given moment, every terminal is in one of the two binary conditions *low* (0) or *high* (1), represented by different voltage levels.
- The logic state of a terminal can, and generally does, change often, as the circuit processes data.
- Logic gates are the building blocks of digital circuits. Combinations of logic gates form circuits designed with specific tasks in mind.
- For example, logic gates are combined to form circuits to add binary numbers (adders), set and reset bits of memory (flip flops), multiplex multiple inputs, etc.
- There are seven basic logic gates: **AND**, **OR**, **XOR**, **NOT**, **NAND**, **NOR**, and **XNOR**.


Truth Table

- A truth table is a good way to show the function of a logic gate. It shows the output states for every possible combination of input states. The symbols 0 (false) and 1 (true) are usually used in truth tables.

Logic Gate Symbols


Inputs and outputs

 - Gates have two or more inputs, except a NOT gate which has only one input. All gates have only one output. Usually the letters A, B, C and so on are used to label inputs, and Q is used to label the output. On this page the inputs are shown on the left and the output on the right.




The inverting circle (o)

 - Some gate symbols have a circle on their output which means that their function includes **inverting** of the output. It is equivalent to feeding the output through a NOT gate. For example the NAND (Not AND) gate symbol shown on the right is the same as an AND gate symbol but with the addition of an inverting circle on the output.





Basic logic gates



- Not

 


- And

  


- Or

  


- Nand

 

- Nor

 


- Xor

 

AND

 - The AND gate requires two inputs and has one output.
- The AND gate only produces an output of 1 when BOTH the inputs are a 1, otherwise the output is 0.




AND

X	Y	Z = X . Y
0	0	0
0	1	0
1	0	0
1	1	1

OR

 - The OR gate has two input lines and one output line. Basically, if either or both of the inputs are a 1, the resulting output value is a 1. Note in the truth table, the only time the output is 0 is when both




OR

X	Y	Z = X + Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT

- The NOT gate is also known as an inverter, simply because it changes the input to its opposite (inverts it).
- The NOT gate accepts only one input and the output is the opposite of the input. In other words, a low-voltage input (0) is converted to a high-voltage output (1). It's that simple!
- A common way of using the NOT gate is to simply attach the circle to the front of another gate. This simplifies the circuit drawing and simply says: "Invert the output from this gate."

 


NOT

X	Z = \bar{X}
0	1
1	0

- The NAND and NOR gates possess a special property: they are **universal**. That is, given enough gates, either type of gate is able to mimic the operation of *any* other gate type. Combinations of them can be used to accomplish any of the basic operations and can thus produce an inverter, an OR gate or an AND gate.

NAND

 
- This is an AND gate with the output inverted, as shown by the 'o' on the output.
- The output is true if input A AND input B are NOT both true: **$Q = \text{NOT (A AND B)}$**
- A NAND gate can have two or more inputs true if NOT all inputs are true.



X	Y	Z = X . Y
0	0	1
0	1	1
1	0	1
1	1	0

NOR

 
- This is an OR gate with the output inverted, as shown by the 'o' on the output. The output Q is true if NOT inputs A OR B are true: **$Q = \text{NOT (A OR B)}$**
- A NOR gate can have two or more inputs true if no inputs are true.



X	Y	Z = $\bar{X} + \bar{Y}$
0	0	1
0	1	0
1	0	0
1	1	0

XOR

 - The output Q is true if either input A is true OR input B is true, **but not when both of them are true: $Q = (A \text{ AND NOT } B) \text{ OR } (B \text{ AND NOT } A)$**
- This is like an OR gate but excluding both inputs being true.
- The output is true if inputs A and B are **DIFFERENT**. EX-OR gates can only have 2 inputs.




XOR

X	Y	Q
0	0	0
0	1	1
1	0	1
1	1	0

XNOR

 - This is an EX-OR gate with the output inverted, as shown by the 'o' on the output.
- The output Q is true if inputs A and B are the **SAME** (both true or both false): **$Q = (A \text{ AND } B) \text{ OR } (\text{NOT } A \text{ AND NOT } B)$**
- EX-NOR gates can only have 2 inputs.



XNOR

X	Y	Q
0	0	1
0	1	0
1	0	0
1	1	1

Basic Boolean Identities


- As with algebra, there will be Boolean operations that we will want to simplify
 - We apply the following Boolean identities to help
 - For instance, in algebra, $x = y * (z + 0) + (z * 0)$ can be simplified to just $x = y * z$

Identity Name	AND Form	OR Form
Identity Law	$1x = x$	$0+x = x$
Null (or Dominance) Law	$0x = 0$	$1+x = 1$
Idempotent Law	$xx = x$	$x+x = x$
Inverse Law	$x\bar{x} = 0$	$x+\bar{x} = 1$
Commutative Law	$xy = yx$	$x+y = y+x$
Associative Law	$(xy)z = x(yz)$	$(x+y)+z = x+(y+z)$
Distributive Law	$x+yz = (x+y)(x+z)$	$x(y+z) = xy+xz$
Absorption Law	$x(x+y) = x$	$x+xy = x$
DeMorgan's Law	$(\overline{xy}) = \bar{x}+\bar{y}$	$(\bar{x}+\bar{y}) = \overline{xy}$
Double Complement Law	$\overline{\bar{x}} = x$	

Commutative


Commutative property of addition

$$A + B = B + A$$

 

Commutative property of multiplication


$$AB = BA$$

 

Associative


Associative property of addition

$$A + (B + C) = (A + B) + C$$

 


Associative property of multiplication

$$A(BC) = (AB)C$$

 


Simplification

$$\mathbf{A + AB = A}$$

 

$$\begin{array}{l} A + AB \\ \downarrow \text{Factoring } \mathbf{A} \text{ out of both terms} \\ A(1 + B) \\ \downarrow \text{Applying identity } \mathbf{A + 1 = 1} \\ A(1) \\ \downarrow \text{Applying identity } \mathbf{1A = A} \\ A \end{array}$$

$$A + \bar{A}B = A + B$$

 


$$\begin{array}{l}
 A + \bar{A}B \\
 \downarrow \text{Applying the previous rule to expand } \mathbf{A} \text{ term} \\
 \mathbf{A + AB + \bar{A}B} \\
 \downarrow \text{Factoring } \mathbf{B} \text{ out of 2}^{\text{nd}} \text{ and 3}^{\text{rd}} \text{ terms} \\
 A + B(A + \bar{A}) \\
 \downarrow \text{Applying identity } \mathbf{A + \bar{A} = 1} \\
 A + B(1) \\
 \downarrow \text{Applying identity } \mathbf{1A = A} \\
 A + B
 \end{array}$$


Distributive

Distributive property

$$A(B + C) = AB + AC$$

 


$$(A + B)(A + C) = A + BC$$

 


$$\begin{aligned}
 &(A + B)(A + C) \\
 &\quad \downarrow \text{Distributing terms} \\
 &AA + AC + AB + BC \\
 &\quad \downarrow \text{Applying identity } AA = A \\
 &A + AC + AB + BC \\
 &\quad \downarrow \text{Applying rule } A + AB = A \\
 &\quad \quad \text{to the } A + AC \text{ term} \\
 &A + AB + BC \\
 &\quad \downarrow \text{Applying rule } A + AB = A \\
 &\quad \quad \text{to the } A + AB \text{ term} \\
 &A + BC
 \end{aligned}$$

DeMorgan's


DeMorgan's Theorems

 


NAND to Negative-OR

 

NOR to Negative-AND

 

... is equivalent to ...

 

$$\overline{AB} = \overline{A} + \overline{B}$$

Practice:

1. Demonstrate by means of truth tables the validities of the following identities:

a. $(XYZ)' = X' + Y' + Z'$

b. $X + YZ = (X + Y)(X + Z)$

c. $X'Y + Y'Z + X'Z = XY' + YZ' + X'Z$

2. Prove the following identity of each of the following Boolean equations using algebraic manipulation:

a. $A'B + B'C' + AB + B'C = 1$

b. $Y + X'Z + XY' = X + Y + Z$

c. $AB + BC'D' + A'BC + C'D = B + C'D$

Karnaugh Map

Minterms – Sum of Product (SOP)

- A product term in which all the variables appear exactly once (complemented or uncomplemented)
- The combination has the value 1
- E.g.: the four minterms for two variables, X and Y are $X'Y'$, $X'Y$, XY' and XY .

- A Boolean function can be represented algebraically from a given truth table by forming the logical sum of all the minterms that produce 1 in the function.

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- Expressed algebraically:

$$F = X'Y'Z' + X'YZ' + XY'Z + XYZ = m_0 + m_2 + m_5 + m_7$$

- In abbreviated form:

$$F(X, Y, Z) = \Sigma m(0, 2, 5, 7)$$

Maxterms – Product of Sum (POS)

- A sum term that contains all the variables in complemented or uncomplemented form
- The combination has the value of 0
- E.g.: the four minterms for two variables, X and Y are $X' + Y'$, $X' + Y$, $X + Y'$ and $X + Y$.

- A boolean function can be represented algebraically from a given truth table by forming the logical sum of all the maxterms that produce 0 in the function.

X	Y	Z	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

- Expressed algebraically:

$$F = (X + Y + Z')(X + Y' + Z')(X' + Y + Z)(X' + Y' + Z) = m_1 + m_3 + m_4 + m_6$$

- Abbreviated form:

$$F(X, Y, Z) = \prod M(1, 3, 4, 6)$$


Karnaugh Maps (K-maps)

- A K-map is a collection of squares
 - Each square represents a minterm
 - The collection of squares is a graphical representation of a Boolean function
 - Adjacent squares differ in the value of one variable
 - Alternative algebraic expressions for the same function are derived by recognizing patterns of squares
- The K-map can be viewed as
 - A reorganized version of the truth table
 - A topologically-warped Venn diagram as used to visualize sets in algebra of sets


Karnaugh Maps - Rules of Simplification

- The Karnaugh map uses the following rules for the simplification of expressions by *grouping* together adjacent cells containing *ones*

 1. Groups may not include any cell containing a zero







 2. Groups may be horizontal or vertical, but not diagonal.



- Groups must contain 1, 2, 4, 8, or in general 2^n cells. That is if $n = 1$, a group will contain two 1's since $2^1 = 2$.

    3. Grouping of 1 should be in 2^n . i.e. grouping should be in 1, 2's, 4's, 8's and so forth.



4. Each group should be as large as possible.

$\backslash AB$	00	01	11	10
C				
0	1	1	1	1
1	0	0	1	1

RIGHT ✓

$\backslash AB$	00	01	11	10
C				
0	1	1	1	1
1	0	0	1	1

WRONG ✗

(Note that no Boolean laws broken,
but not sufficiently minimal)

5. Each cell containing a *one* must be in at least one group.


AB \ C	00	01	11	10
0	0	0	1	1
1	0	0	0	1

Group I


Group II

1 present in at least one group.

6. Groups may overlap

 

 7. Groups may wrap around the table. The leftmost cell in a row may be grouped with the rightmost cell and the top cell in a column may be grouped with the bottom cell.



8. There should be as few groups as possible, as long as this does not contradict any of the previous rules.

$\begin{array}{c} \diagdown \\ AB \\ C \end{array}$	00	01	11	10
0	1	1	1	1
1	0	0	1	1


RIGHT ✓

$\begin{array}{c} \diagdown \\ AB \\ C \end{array}$	00	01	11	10
0	1	1	1	1
1	0	0	1	1


WRONG ✗

Re-arranging the truth table

 - A two-variable function has four possible minterms. We can re-arrange these minterms into a **Karnaugh map**.



 - Now we can easily see which minterms contain common literals.
 - Minterms on the left and right sides contain y' and y respectively.
 - Minterms in the top and bottom rows contain x' and x respectively.



- Imagine a two-variable sum of minterms:

$$x'y' + x'y$$

- Both of these minterms appear in the top row of a Karnaugh map, which means that they both contain the literal x' .

		y
	x'y'	x'y
x	xy'	xy

- What happens if you simplify this expression using Boolean algebra?

$$\begin{aligned}
 x'y' + x'y &= x'(y' + y) && [\text{Distributive}] \\
 &= x' \bullet 1 && [y + y' = 1] \\
 &= x' && [x \bullet 1 = x]
 \end{aligned}$$

- Another example expression is $x'y + xy$.
 - Both minterms appear in the right side, where y is uncomplemented.
 - Thus, we can reduce $x'y + xy$ to just y .

		y
	x'y'	x'y
x	xy'	xy

- How about $x'y' + x'y + xy$?
 - We have $x'y' + x'y$ in the top row, corresponding to x' .
 - There's also $x'y + xy$ in the right side, corresponding to y .
 - This whole expression can be reduced to $x' + y$.

		y
	x'y'	x'y
x	xy'	xy

Three-variable Karnaugh map

- For a three-variable expression with inputs x , y , z , the arrangement of minterms is more tricky:

		YZ			
		00	01	11	10
X	0	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
	1	$xy'z'$	$xy'z$	xyz	xyz'

		YZ			
		00	01	11	10
X	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

- Another way to label the K-map (use whichever you like):

		y			
		$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
X	$xy'z'$	$xy'z$	xyz	xyz'	
	z				

		y			
		m_0	m_1	m_3	m_2
X	m_4	m_5	m_7	m_6	
	z				

- With this ordering, any group of 2, 4 or 8 adjacent squares on the map contains common literals that can be factored out.

		y		
	x'y'z'	x'y'z	x'yz	x'yz'
x	xy'z'	xy'z	xyz	xyz'
		z		

$$\begin{aligned}
 & x'y'z + x'yz \\
 = & x'z(y' + y) \\
 = & x'z \bullet 1 \\
 = & x'z
 \end{aligned}$$

- “Adjacency” includes wrapping around the left and right sides:

		y		
	x'y'z'	x'y'z	x'yz	x'yz'
x	xy'z'	xy'z	xyz	xyz'
		z		

$$\begin{aligned}
 & x'y'z + x'yz' + x'yz + xyz' \\
 = & z'(x'y' + xy' + x'y + xy) \\
 = & z'(y'(x' + x) + y(x' + x)) \\
 = & z'(y' + y) \\
 = & z'
 \end{aligned}$$

- We'll use this property of adjacent squares to do our simplifications.

- Three variables maps exhibit the following characteristics:
 - One square represents a minterm of three literals
 - A rectangle of two squares represents a product term of two literals (or variables)
 - A rectangle of four squares represents a product term of one literal (or variable)
 - A rectangle of eight squares encompasses the entire map and produces a function that is always equal to logic 1.

Example K-map simplification


- Let's consider simplifying $f(x,y,z) = xy + y'z + xz$.
- First, you should convert the expression into a sum of minterms form, if it's not already.
 - The easiest way to do this is to make a truth table for the function, and then read off the minterms.
 - You can either write out the literals or use the minterm shorthand.
- Here is the truth table and sum of minterms for our example:

x	y	z	$f(x,y,z)$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$\begin{aligned}f(x,y,z) &= x'y'z + xy'z + xyz' + xyz \\ &= m_1 + m_5 + m_6 + m_7\end{aligned}$$


K-maps from truth tables

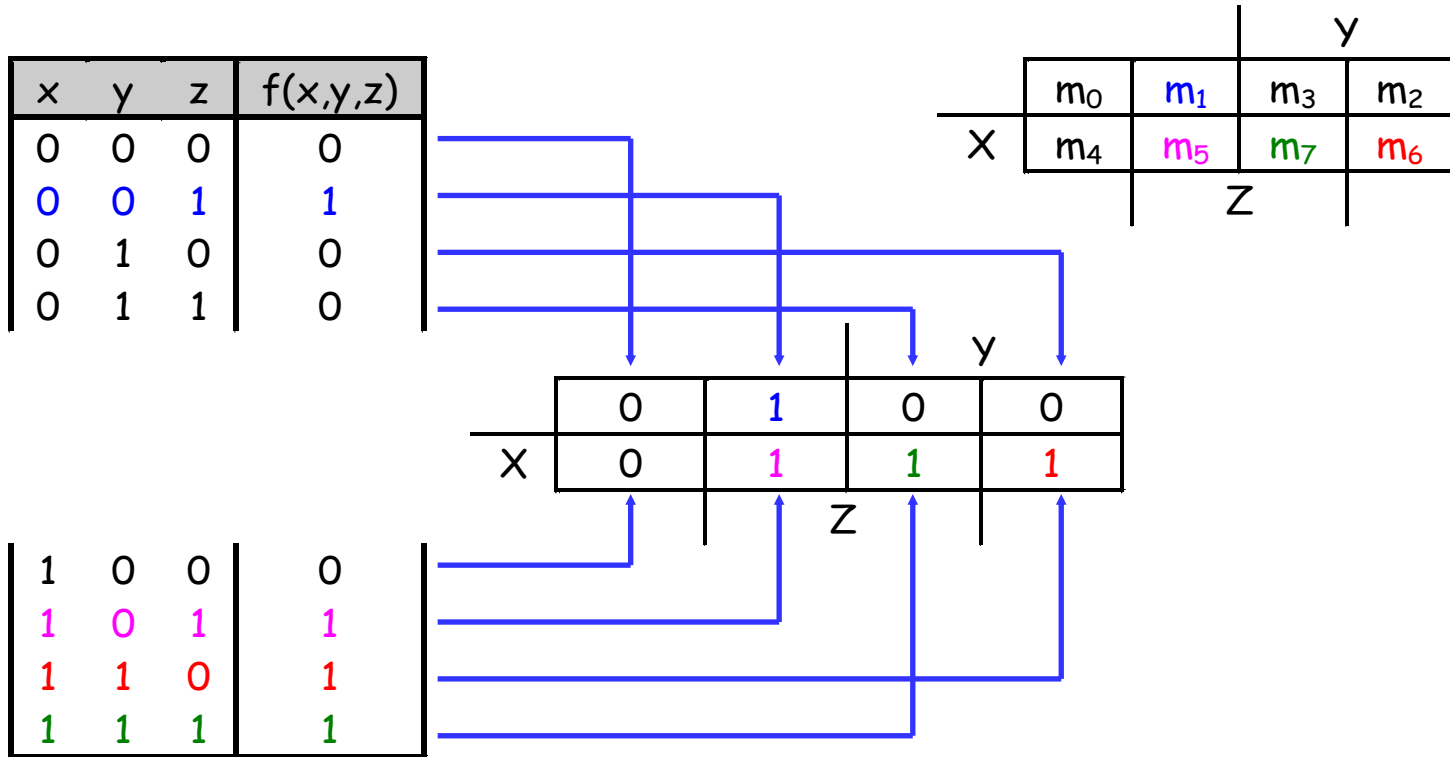- You can also fill in the K-map directly from a truth table.
 - The output in row i of the table goes into square m_i of the K-map.
 - Remember that the rightmost columns of the K-map are “switched.”



Grouping the minterms together

 - The most difficult step is grouping together all the 1s in the K-map.
 - Make **rectangles** around groups of one, two, four or eight 1s.
 - All of the 1s in the map should be included in at least one rectangle.
 - Do *not* include any of the 0s.



- Each group corresponds to one product term. For the simplest result:
 - Make as few rectangles as possible, to minimize the number of products in the final expression.
 - Make each rectangle as large as possible, to minimize the number of literals in each term.
 - It's all right for rectangles to overlap, if that makes them larger.

Four-variable K-maps

- We can do four-variable expressions too!
 - The minterms in the third and fourth columns, *and* in the third and fourth rows, are switched around.
 - Again, this ensures that adjacent squares have common literals.

		y		
	w'x'y'z'	w'x'y'z	w'x'yz	w'x'yz'
	w'xy'z'	w'xy'z	w'xyz	w'xyz'
w	wxy'z'	wxy'z	wxyz	wxyz'
	wx'y'z'	wx'y'z	wx'yz	wx'yz'
		z		x

		y		
	m ₀	m ₁	m ₃	m ₂
	m ₄	m ₅	m ₇	m ₆
w	m ₁₂	m ₁₃	m ₁₅	m ₁₄
	m ₈	m ₉	m ₁₁	m ₁₀
		z		x

- Grouping minterms is similar to the three-variable case, but:
 - You can have rectangular groups of 1, 2, 4, 8 or 16 minterms.
 - You can wrap around *all four* sides.

- Four variables maps exhibit the following characteristics:
 - A rectangle of 2 squares represents a product term of three literals (or variables)
 - A rectangle of 4 squares represents a product term of two literals (or variables)
 - A rectangle of 8 squares represents a product term of one literal (or variable)
 - A rectangle of 4 squares produces a function that is always equal to logic 1

Don't Care Conditions

- In a Kmap, a don't care condition is identified by an X in the cell of the minterm(s) for the don't care inputs, as shown below.
- In performing the simplification, we are free to include or ignore the X 's when creating our groups.

	YZ	00	01	11	10
WX					
00		X	1	1	X
01			X	1	
11		X		1	
10				1	

Don't Care Conditions

- In one grouping in the Kmap below, we have the function:

$$F(W, X, Y, Z) = \bar{W}\bar{X} + YZ$$

WX \ YZ	YZ			
	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

Don't Care Conditions

- A different grouping gives us the function:

$$F(W, X, Y, Z) = \bar{W}Z + YZ$$

WX \ YZ	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

The table shows a 4x4 Karnaugh map for the function F(W, X, Y, Z). The rows are labeled WX and the columns are labeled YZ. The cells contain values: 00 (X), 01 (1), 11 (1), 10 (X) for WX=00; 01 (X), 11 (1) for WX=01; 00 (X), 11 (1) for WX=11; and 11 (1) for WX=10. A pink box highlights the 2x2 group of cells (01, 11) for WX=00 and (01, 11) for WX=01. A green box highlights the 4x1 group of cells (11, 10) for WX=00, (11) for WX=01, (11) for WX=11, and (11) for WX=10.

Don't Care Conditions

- The truth table of:

$$F(W, X, Y, Z) = \bar{W}\bar{X} + YZ$$

is different from the truth table of:

$$F(W, X, Y, Z) = \bar{W}Z + YZ$$

- However, the values for which they differ, are the inputs for which we have don't care conditions.

WX \ YZ	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

WX \ YZ	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	